

## Capacitance

---

### Capacitance

A capacitor is any device used to store charge. The capacitance of an isolated conductor is the ratio of charge stored to the change in electric potential.

$$\text{capacitance, } C = \frac{Q}{V} \text{ unit: Farad, F}$$

$$\text{For a parallel plate capacitor, } C = \frac{\epsilon_0 \epsilon_r A}{d}$$

---

### Energy stored

Charging a capacitor means transferring charge from the plate at lower potential to the plate at higher potential, which requires energy. Thus work done in charging = energy stored.

If a capacitor is charged to  $V$  by  $Q$  then the area under a  $V$ - $Q$  graph gives the work done.

$$\text{Work done, } W = \frac{1}{2} QV = \frac{1}{2} CV^2 = \frac{1}{2} \frac{Q^2}{C}$$

---

### Discharging

Charge left on a capacitor  $t$  s after it starts discharging,  $Q = Q_0 e^{-\frac{t}{RC}}$

For a discharging capacitor the graphs of charge, voltage and current against time all have the same shape, so this formula works for  $V$  and  $I$  too.

The **time constant** is  $t$  taken for  $Q$  to fall to  $\frac{1}{e}$  of its previous value.  $T = RC$

From this, we can calculate that the time for charge or voltage to half in value is  $0.693RC$ .

---

### Charging

The rate of charge leaving from or arriving on a capacitor depends on how much charge is already there. More work needs to be done to push electrons onto a partially charged capacitor than an empty one.

$$\text{For a charging capacitor, } Q = Q_0(1 - e^{-\frac{t}{RC}})$$

The graphs of  $Q$  and  $V$  against  $t$  show that charge & voltage increase rapidly at first, but the rate of change decreases as a maximum is approached. This means this equation

works for V as well as Q, but not I (which looks the same for both a charging and discharging capacitor). Note that these don't work if current is kept constant.

Increasing R leads to a shallower charging or discharging curve which takes longer to reach its maximum or minimum. R decreases the current - decreasing the rate of flow of charge.

$$I = \frac{Q}{t}$$

---

### **Polarised molecules**

Some molecules have one part more positive and another more negative - they are polarised.

If a polarised molecule is placed in an electric field, the two ends respond differently to the field, moving in opposite directions, rotating the molecule until it lines up with the field.